



Grupo 1, Lab 3

Lucas Pinto

Carlos Vidal


Assignment 1 – Hadamard codes

The challenge is to design a solution for an encoder and a decoder that implements a combinatorial algorithm for message transmission with the error correcting properties developed by Richard Hamming using Hadamard codes of class $[8, 4, 4]_2$, described as $[n, k, d]$, where n =blocklength, k =message length and d =minimum distance, or $[2^k, K, 2^{k-1}]$.


An additional requirement stipulates that either one, the encoder or the decoder, should implement a serial(series) input, and the other one a parallel input, so our choice was to implement a serial input encoder and a parallel input decoder.

1. Serial input encoder:

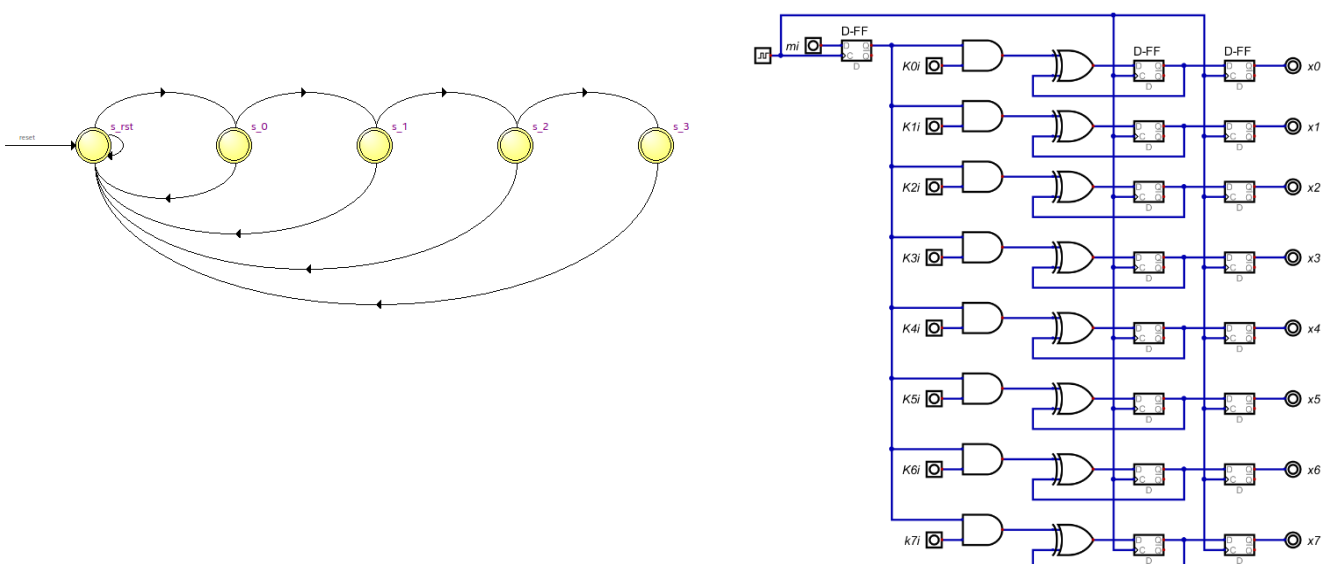1.1. Data flow and serial-parallel control unit implementation



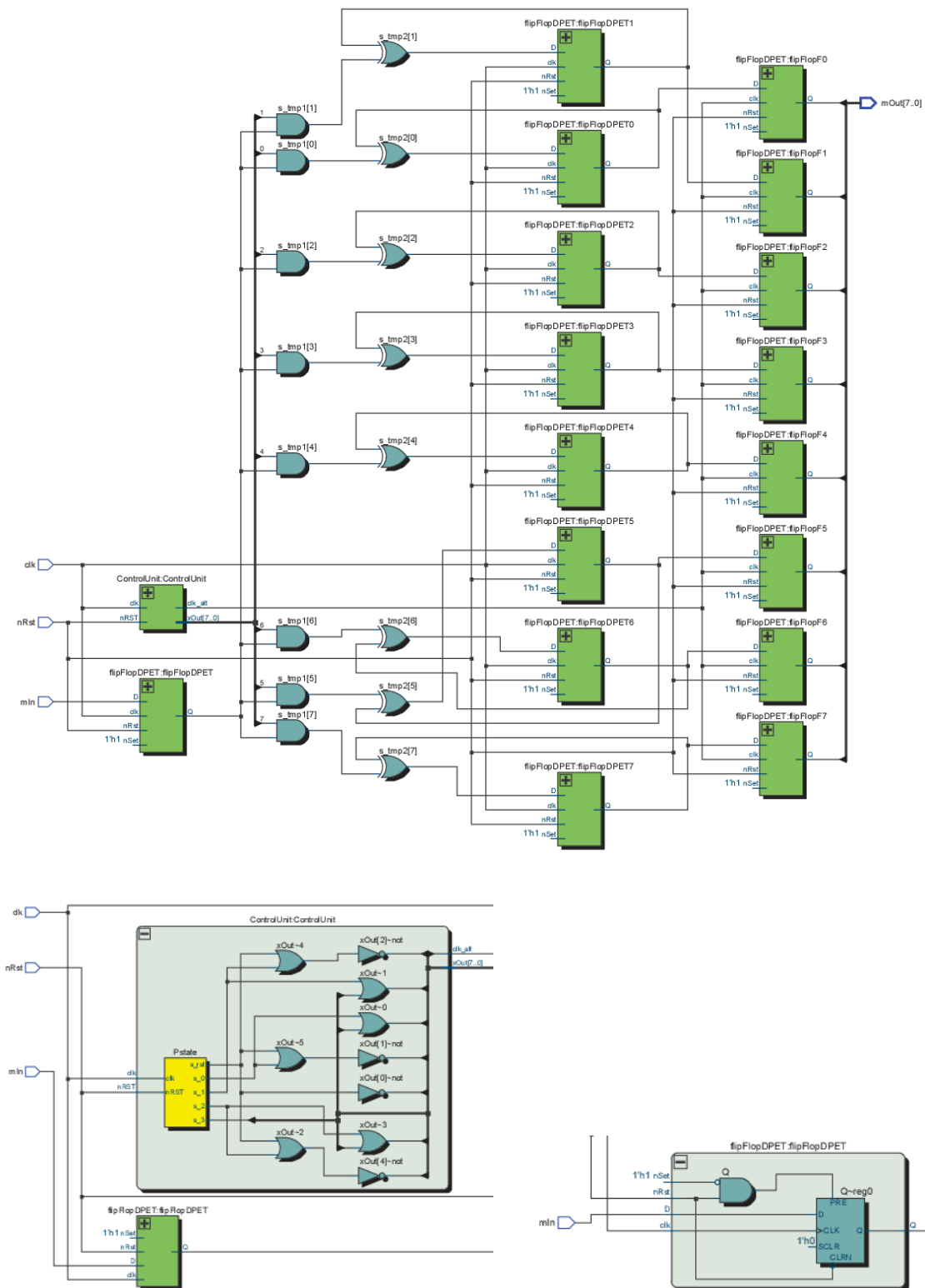
1.2. Circuit interface and schematics of the internal organization:



1.3. Implementation cost:


14 AND gates, 8 XOR gates, 4 NOT gates and 17 D Flip-Flop PET.

 1.4. Quartus project and operation simulation:



2. Parallel input decoder:

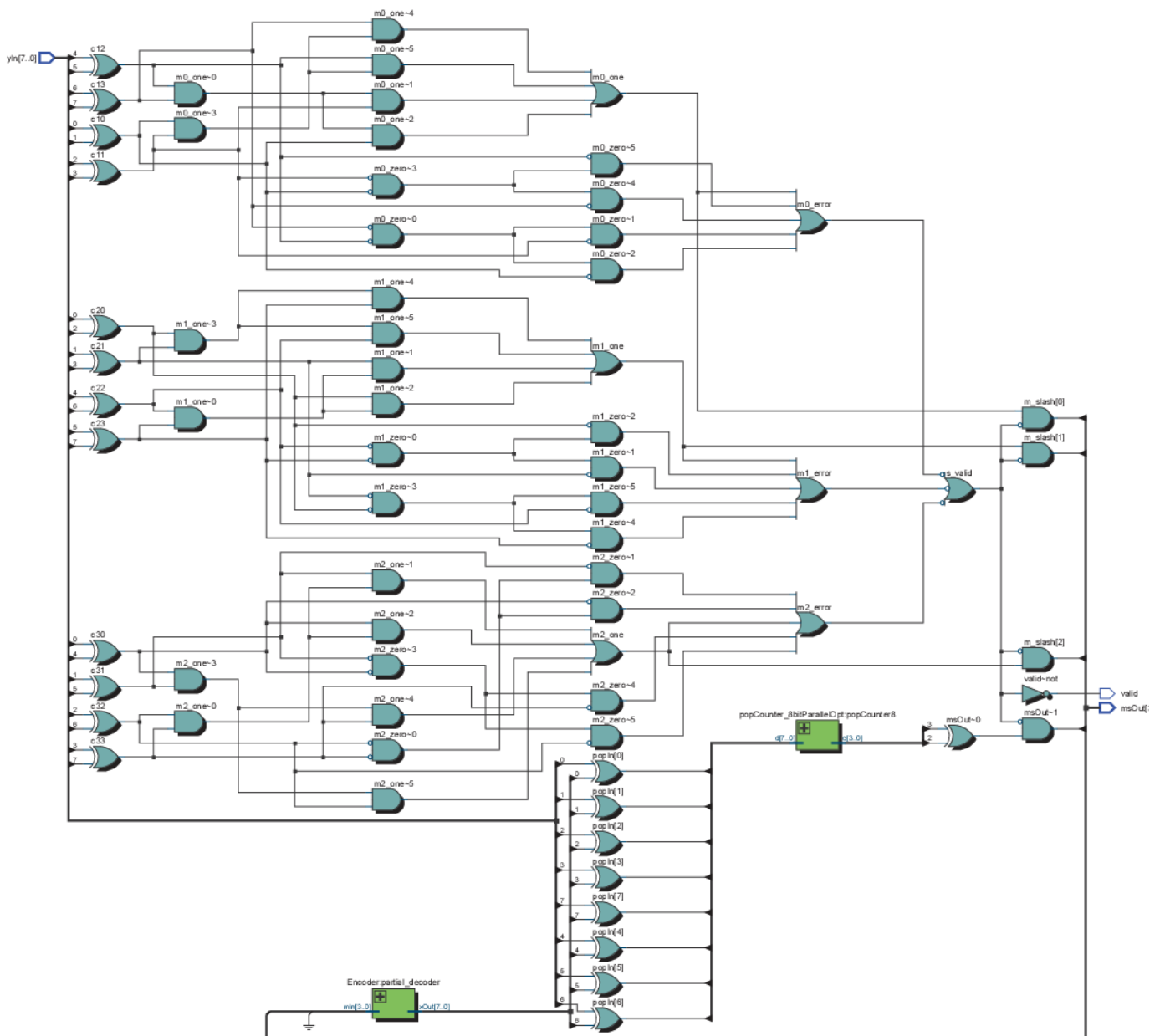2.1 Circuit interface and schematics of the internal organization:



2.2. Implementation cost:

20 XOR, 40 AND, 23 OR, 29 NOT and 1 8-bit POPCounter.

8-bit POPCounter =

$$\begin{aligned}
 &4x(1XOR + 1AND) + \\
 &2x[(1XOR + 1AND) + (2XOR + 1AND)] + \\
 &(1XOR + 1AND) + (2XOR + 2AND + 1OR) + (2XOR + 1AND) = \\
 &= 15XOR + 12AND + 1OR
 \end{aligned}$$

8-bit POPCounter Propagation Delay =

Stage 0: 1XOR gate

Stage 1: 2XOR gates

Stage 2: 2XOR gates + 1AND gate + 1OR gate

Total: 5XOR gates + 1AND gate + 1OR gate

TOTAL COST = 35XOR, 52AND, 24OR, 29NOT

Total Propagation Delay =

m'3 path :

Stage 0: 1XOR gate

Stage 1: 5XOR gates + 1AND gate + 1OR gate (8-bit POPCounter)

Stage 2: 1XOR gates + 1AND gate

Total: 7XOR gates + 2AND gates + 1OR gate

m'0, m'1 and m'2 path worst case:

Stage 0: 1XOR gate + 1AND gate

Stage 1: 1NOT gate + 1AND gate (inverted input AND gate)

Stage 2: 1NOT gate + 1AND gate (inverted input AND gate)

Stage 3: 1OR gate


Stage 4: 1NOT gate + 1OR gate (inverted input OR gate)

Stage 5: 1NOT gate + 1AND gate (inverted input AND gate)

Total: 4NOT gates + 1XOR gate + 4AND gates + 2OR gates

2.3. Quartus project and operation simulation:

Simulation1

 

Simulation2

